


- 5 (a) (i) State Kirchhoff's second law.

.....  
 ..... [1]

- (ii) Kirchhoff's second law is linked to the conservation of a certain quantity. State this quantity.

..... [1]

- (b) The circuit shown in Fig. 5.1 is used to compare potential differences.

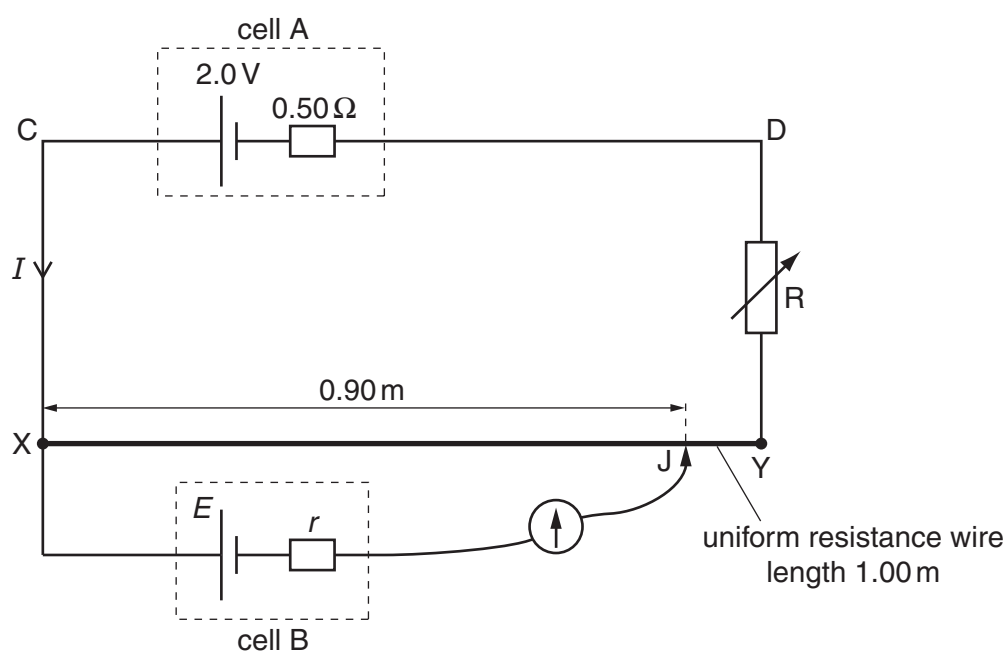

**Fig. 5.1**

The uniform resistance wire XY has length 1.00 m and resistance  $4.0\ \Omega$ . Cell A has e.m.f. 2.0 V and internal resistance  $0.50\ \Omega$ . The current through cell A is  $I$ . Cell B has e.m.f.  $E$  and internal resistance  $r$ .

The current through cell B is made zero when the movable connection J is adjusted so that the length of XJ is 0.90 m. The variable resistor R has resistance  $2.5\ \Omega$ .

- (i) Apply Kirchhoff's second law to the circuit CXYDC to determine the current  $I$ .

$I = \dots\dots\dots$  A [2]

(ii) Calculate the potential difference across the length of wire XJ.

potential difference = ..... V [2]

(iii) your answer in (ii) to state the value of  $E$ .

$E =$  ..... V [1]

(iv) State why the value of the internal resistance of cell B is not required for the determination of  $E$ .

.....  
.....[1]