

5 (a) a cell, explain the terms


(i) *electromotive force (e.m.f.),*

.....  
..... [1]

(ii) *internal resistance.*

.....  
..... [1]

(b) The circuit of Fig. 5.1 shows two batteries A and B and a resistor R connected in series.

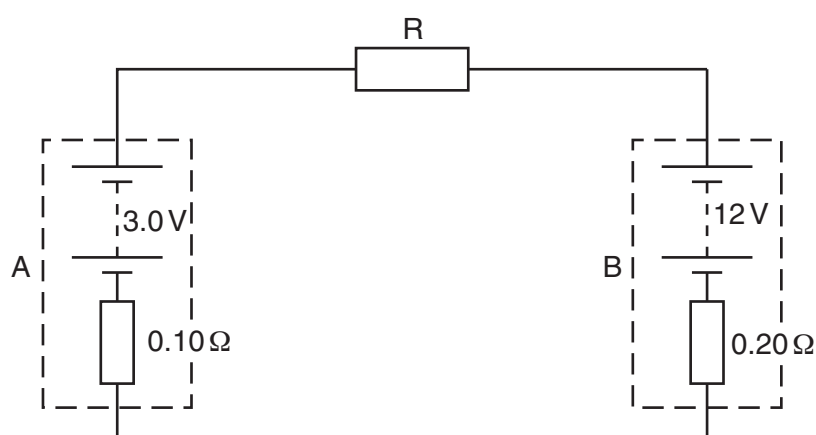

**Fig. 5.1**

Battery A has an e.m.f. of 3.0V and an internal resistance of 0.10Ω. Battery B has an e.m.f. of 12V and an internal resistance of 0.20Ω. Resistor R has a resistance of 3.3Ω.

(i) Apply Kirchhoff's second law to calculate the current in the circuit.

current = ..... A [2]

(ii) Calculate the power transformed by battery B.

power = ..... W [2]

- (iii) Calculate the total energy lost per second in resistor R and the internal resistances.

energy lost per second = .....  $\text{Js}^{-1}$  [2]

- (c) The circuit of Fig. 5.1 may be used to store energy in battery A. Suggest how your answers in (b) support this statement.

.....  
.....  
..... [1]