

- 5 (a) (i) State Kirchhoff's first law.

.....  
..... [1]

- (ii) Kirchhoff's first law is linked to the conservation of a certain quantity. State this quantity.

..... [1]

- (b) A variable resistor of resistance  $R$  is used to control the current in a circuit, as shown in Fig. 5.1.

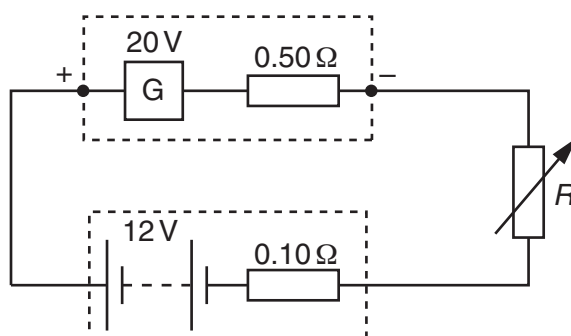


Fig. 5.1

The generator  $G$  has e.m.f.  $20\text{ V}$  and internal resistance  $0.50\ \Omega$ . The battery has e.m.f.  $12\text{ V}$  and internal resistance  $0.10\ \Omega$ . The current in the circuit is  $2.0\text{ A}$ .

- (i) Apply Kirchhoff's second law to the circuit to determine the resistance  $R$ .

$R = \dots\dots\dots\ \Omega$  [2]

- (ii) Calculate the total power generated by  $G$ .

power =  $\dots\dots\dots\text{ W}$  [2]

- (iii) Calculate the power loss in the total resistance of the circuit.

power = ..... W [2]

- (iv) The circuit is used to supply energy to the battery from the generator. Determine the efficiency of the circuit.

efficiency = ..... [2]