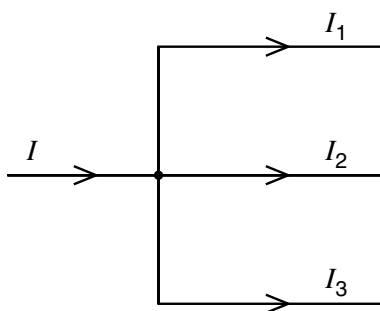


- 33** At a circuit junction, a current I divides into currents I_1 , I_2 and I_3 .



These currents are related by the equation

$$I = I_1 + I_2 + I_3.$$

Which law does this statement illustrate and on what principle is the law based?

- A** Kirchhoff's first law based on conservation of charge
 - B** Kirchhoff's first law based on conservation of energy
 - C** Kirchhoff's second law based on conservation of charge
 - D** Kirchhoff's second law based on conservation of energy
- 34** The combined resistance R_T of two resistors of resistances R_1 and R_2 connected in parallel is given by the formula

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

Which statement is used in the derivation of this formula?

- A** The currents through the two resistors are equal.
- B** The potential difference across each resistor is the same.
- C** The supply current is split between the two resistors in the same ratio as the ratio of their resistances.
- D** The total power dissipated is the sum of the powers dissipated in the two resistors separately.