



Fig. 7.2

Calculate, for $I = 1.2\text{ A}$,

- (i) the p.d. across X,

p.d. = V [2]

- (ii) the resistance of Y,

resistance = Ω [3]

- (iii) the power dissipated in the battery.

power = W [2]

- (c) Fig. 7.2 to explain the variation in the terminal p.d. of the battery as the resistance R of X is increased.

.....
 [1]