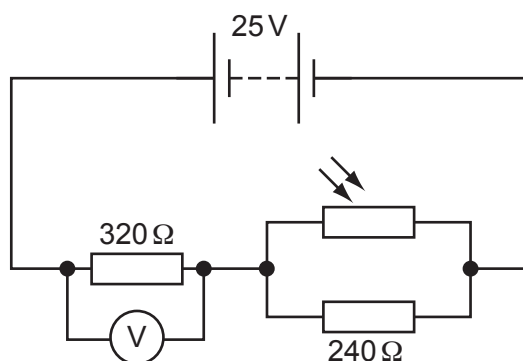


- 6 A battery is connected in a circuit with a light-dependent resistor (LDR), two fixed resistors and a voltmeter, as shown in Fig. 6.1.



**Fig. 6.1**

The battery has an electromotive force (e.m.f.) of 25 V and negligible internal resistance. The resistors have resistances of 320 Ω and 240 Ω.

- (a) The voltmeter displays a reading of 16 V.

- (i) Show that the current in the battery is 0.050 A.

[1]

- (ii) Calculate the resistance of the LDR.

resistance = ..... Ω [3]

(iii) Determine the ratio

$$\frac{\text{power dissipated in the LDR}}{\text{power dissipated in the } 240\,\Omega \text{ resistor}}$$

ratio = ..... [2]

(b) The intensity of the light incident on the LDR increases.

State and explain what happens to the voltmeter reading.

.....  
.....  
.....  
..... [3]

[Total: 9]