
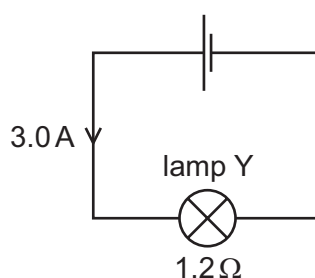


- 30 The current I in a metal wire is given by the expression shown.

$$I = Anvq$$

What does the symbol n represent?

- A the number of atoms per unit volume of the metal
 - B the number of free electrons per atom in the metal
 - C the number of free electrons per unit volume of the metal
 - D the total number of electrons per unit volume of the metal
- 31 The circuit diagrams show two lamps X and Y each connected to a cell. The current in lamp X is 0.50 A and its resistance is $9.6\ \Omega$. The current in lamp Y is 3.0 A and its resistance is $1.2\ \Omega$.

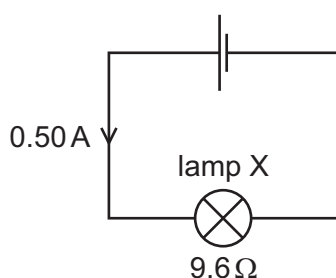

What is the ratio $\frac{\text{power in lamp X}}{\text{power in lamp Y}}$?

- A 0.22
 - B 0.75
 - C 1.3
 - D 4.5
- 32 A cylindrical piece of a soft, electrically-conducting material has resistance R . It is rolled out so that its length is doubled but its volume stays constant.

What is its new resistance?

- A $\frac{R}{2}$
- B R
- C $2R$
- D $4R$

- 33 The sum of the electrical currents into a point in a circuit is equal to the sum of the currents out of the point.

Which statement is correct?

- A This is Kirchhoff's first law, which results from the conservation of charge.
- B This is Kirchhoff's first law, which results from the conservation of energy.
- C This is Kirchhoff's second law, which results from the conservation of charge.
- D This is Kirchhoff's second law, which results from the conservation of energy.