

- 5 (a) State Kirchhoff's second law.


.....

.....

.....

.....[2]


- (b) A battery is connected in parallel with two lamps A and B, as shown in Fig. 5.1.

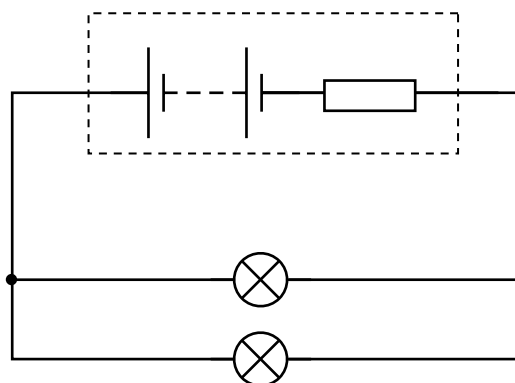

**Fig. 5.1**

The battery has electromotive force (e.m.f.) 6.8V and internal resistance  $r$ .

The  $I$ – $V$  characteristics of lamps A and B are shown in Fig. 5.2.

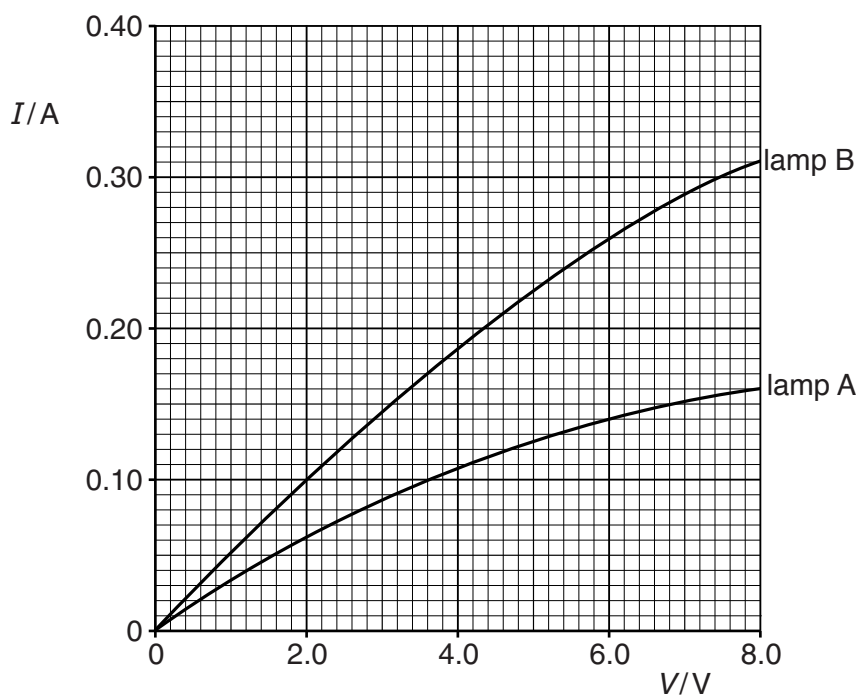

**Fig. 5.2**

The potential difference across the battery terminals is 6.0V.

- (i) Fig. 5.2 to show that the current in the battery is 0.40 A.

[2]

- (ii) Calculate the internal resistance  $r$  of the battery.

$r = \dots\dots\dots \Omega$  [2]

- (iii) Determine the ratio

$$\frac{\text{resistance of lamp A}}{\text{resistance of lamp B}}.$$

ratio =  $\dots\dots\dots$  [2]

(iv) Determine

1. the total power produced by the battery,

power = ..... W [2]

2. the efficiency of the battery in the circuit.

efficiency = ..... [2]

[Total: 12]