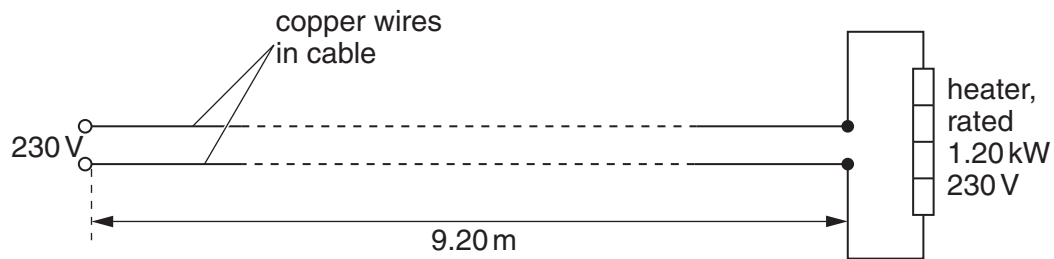


- 8 An electric heater has a constant resistance and is rated as 1.20 kW, 230 V.

The heater is connected to a 230 V supply by means of a cable that is 9.20 m long, as illustrated in Fig. 8.1.



**Fig. 8.1**

The two copper wires that make up the cable each have a circular cross-section of diameter 0.900 mm. The resistivity of copper is  $1.70 \times 10^{-8} \Omega \text{ m}$ .

**(a)** Show that

- (i)** the resistance of the heater is  $44.1 \Omega$ ,

[2]

- (ii)** the total resistance of the cable is  $0.492 \Omega$ .

[2]