

- 30 An electrical conductor has a resistance of $5.6\text{ k}\Omega$. A potential difference (p.d.) of 9.0 V is applied across its ends.

How many electrons pass a point in the conductor in one minute?

- A 6.0×10^{20} B 1.0×10^{19} C 6.0×10^{17} D 1.0×10^{16}

- 31 A fixed resistor of resistance 12Ω is connected to a battery. There is a current of 0.20 A in the resistor. The current is now doubled.

What is the new power dissipated in the resistor?

- A 0.48 W B 0.96 W C 1.92 W D 4.8 W

- 32 Which **measurements** are taken in order to calculate the resistivity of the metal of a piece of wire?

- A p.d., current, area, length
B p.d., current, diameter, length
C resistance, area, length
D resistance, length, radius

- 33 A 12 V battery is charged for 20 minutes by connecting it to a source of electromotive force (e.m.f.). The battery is supplied with $7.2 \times 10^4\text{ J}$ of energy in this time.

How much charge flows through the battery?

- A 5.0 C B 60 C C 100 C D 6000 C