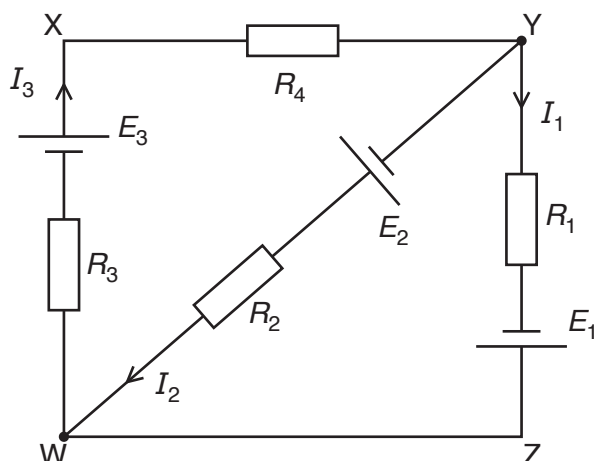


- 5 Three cells of electromotive forces (e.m.f.)  $E_1$ ,  $E_2$  and  $E_3$  are connected into a circuit, as shown in Fig. 5.1.



**Fig. 5.1**

The circuit contains resistors of resistances  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ . The currents in the different parts of the circuit are  $I_1$ ,  $I_2$  and  $I_3$ . The cells have negligible internal resistance.

Kirchhoff's laws to state an equation relating

- (a)  $I_1$ ,  $I_2$  and  $I_3$ ,

.....[1]

- (b)  $E_1$ ,  $E_3$ ,  $R_1$ ,  $R_3$ ,  $R_4$ ,  $I_1$  and  $I_3$  in loop WXYZW,

.....  
 .....[1]

- (c)  $E_1$ ,  $E_2$ ,  $R_1$ ,  $R_2$ ,  $I_1$  and  $I_2$  in loop YZWY.

.....  
 .....[1]

[Total: 3]