

4 (a) The output of a heater is 2.5 kW when connected to a 220 V supply.

(i) Calculate the resistance of the heater.

resistance = .....  $\Omega$  [2]

(ii) The heater is made from a wire of cross-sectional area  $2.0 \times 10^{-7} \text{ m}^2$  and resistivity  $1.1 \times 10^{-6} \Omega \text{ m}$ .

your answer in (i) to calculate the length of the wire.

length = ..... m [3]

(b) The supply voltage is changed to 110 V.

(i) Calculate the power output of the heater at this voltage, assuming there is no change in the resistance of the wire.

power = ..... W [1]

(ii) State and explain quantitatively **one** way that the wire of the heater could be changed to give the same power as in (a).

.....  
.....  
..... [2]