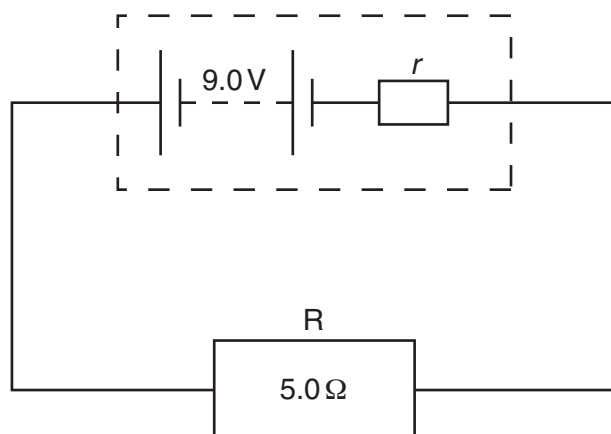


- 6 A battery connected in series with a resistor  $R$  of resistance  $5.0\ \Omega$  is shown in Fig. 6.1.



**Fig. 6.1**

The electromotive force (e.m.f.) of the battery is  $9.0\text{V}$  and the internal resistance is  $r$ .  
The potential difference (p.d.) across the battery terminals is  $6.9\text{V}$ .

- (a) energy considerations to explain why the p.d. across the battery is not equal to the e.m.f. of the battery.

.....  
 .....  
 ..... [2]

- (b) Calculate

- (i) the current in the circuit,

current = ..... A [2]

- (ii) the internal resistance  $r$ .

$r =$  .....  $\Omega$  [2]

(c) Calculate, for the battery in the circuit,

(i) the total power produced,

power = ..... W [2]

(ii) the efficiency.

efficiency = ..... [2]