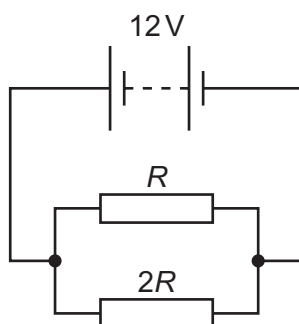


- 30** A metal wire is connected between the terminals of a cell so that there is a current in the wire.

Which statement is correct?

- A** Negatively charged electrons in the wire move from the negative terminal to the positive terminal.
  - B** Negatively charged nuclei in the wire move from the negative terminal to the positive terminal.
  - C** Positively charged electrons in the wire move from the positive terminal to the negative terminal.
  - D** Positively charged nuclei in the wire move from the positive terminal to the negative terminal.
- 31** Two resistors of resistances  $R$  and  $2R$  are connected in parallel with a battery of electromotive force (e.m.f.)  $12\text{ V}$  and negligible internal resistance.



The total power dissipated by the two resistors is  $36\text{ W}$ .

What is the value of  $R$ ?

- A**  $0.50\ \Omega$
  - B**  $2.7\ \Omega$
  - C**  $4.0\ \Omega$
  - D**  $6.0\ \Omega$
- 32** A wire has a length of  $3.0\text{ m}$  and is made of metal of resistivity  $4.9 \times 10^{-7}\ \Omega\text{ m}$ .

A potential difference (p.d.) of  $12\text{ V}$  is applied across the wire so that it has a current of  $1.4\text{ A}$ .

What is the cross-sectional area of the wire?

- A**  $1.2 \times 10^{-7}\text{ m}^2$
- B**  $1.7 \times 10^{-7}\text{ m}^2$
- C**  $1.1 \times 10^{-6}\text{ m}^2$
- D**  $1.3 \times 10^{-5}\text{ m}^2$