


- 30 The current I in a conductor is given by the equation shown.

$$I = Anvq$$

What does the letter n represent in this equation?

- A charge carried per charge carrier
 - B number of charge carriers per unit area
 - C number of charge carriers per unit volume
 - D total mass of charge carriers per unit volume
- 31 In the circuit shown, the battery has an electromotive force (e.m.f.) of 6.0 V and negligible internal resistance.

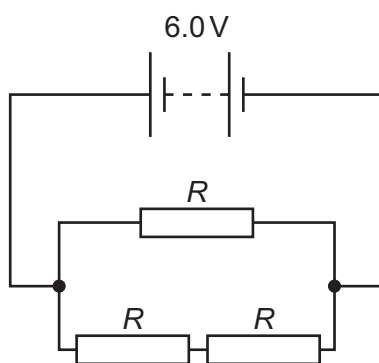The three resistors each have resistance R .



The total power dissipated in the resistor network is 24 W.

What is the value of R ?

- A $0.50\ \Omega$ B $1.0\ \Omega$ C $1.5\ \Omega$ D $2.3\ \Omega$
- 32 Which graph could show how the resistance R of a filament lamp varies with the applied potential difference (p.d.) V , as V is increased to the normal operating p.d.?

