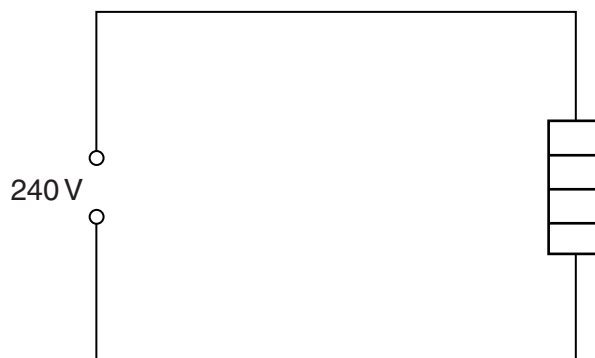


- 6 (a) Define *potential difference* (p.d.).

.....[1]

- (b) A power supply of e.m.f. 240V and zero internal resistance is connected to a heater as shown in Fig. 6.1.



**Fig. 6.1**

The wires used to connect the heater to the power supply each have length 75m. The wires have a cross-sectional area  $2.5\text{mm}^2$  and resistivity  $18\text{n}\Omega\text{m}$ . The heater has a constant resistance of  $38\Omega$ .

- (i) Show that the resistance of each wire is  $0.54\Omega$ .

[3]

- (ii) Calculate the current in the wires.

current = ..... A [3]

- (iii) Calculate the power loss in the wires.

power = ..... W [3]

- (c) The wires to the heater are replaced by wires of the same length and material but having a cross-sectional area of  $0.50 \text{ mm}^2$ . Without further calculation, state and explain the effect on the power loss in the wires.

.....

.....

.....[2]